

VICTORIA

UNIVERSITY OF WELLINGTON

TE WHARE WĀNANGA
O TE ŪPOKO O TE IKA A MĀUI



ENGR142 2020, 2nd Trimester

Lecturers: B. Ruck, P. Galvosas, and C. Hollitt

Name	
ID	


Problem	1	2	Σ
Marks			

Final test 20th October, 2020

Problem 1: DC circuits

(20 Marks)

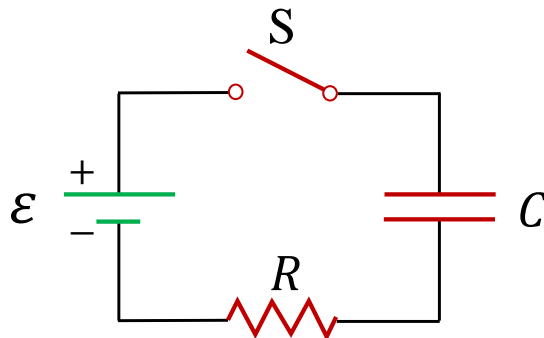- (a) The circuit below shows an RC circuit that is to be connected to the battery at time $t = 0$.



- (a.1) Using Kirchhoff's rules find the governing differential equation for the circuit in the figure after the switch has been closed. You may use Q/C for the voltage drop across the capacitor.

[4 marks]

- (a.2) By inserting it into the differential equation you derived in (a.1), show that

$$Q(t) = \epsilon C \left(1 - e^{-\frac{t}{RC}}\right)$$

describes how the current varies with time.

[4 marks]

- (a.3) When using a battery of emf ε to build up current I in an inductor in series with a resistor R , application of Kirchhoff's loop rule gives

$$\varepsilon - IR - L \frac{dI}{dt} = 0,$$

which has a solution

$$I(t) = \frac{\varepsilon}{R} \left(1 - e^{-\frac{R}{L}t}\right).$$

Draw the corresponding circuit diagram and comment on similarities and differences between this RL circuit and the RC circuit above and its current.

[4 marks]

- (a.4) By relating Faraday's law to the magnetic flux created by the current through a coil, explain how an emf is induced through self-inductance. You may either use equations or explain in words.

[4 marks]

- (b) Consider a 1.0 metre long Nichrome wire with a radius of 0.5 cm. The electrical resistivity of Nichrome is $1.0 \times 10^{-6} \Omega\text{m}$.

- (b.1) What would happen to the *electrical resistance* of the Nichrome wire if its length was doubled?

[1 mark]

- (b.2) What would happen to the *electrical resistivity* of the Nichrome wire if its length was doubled?

[1 mark]

- (b.3) What would happen to the *electrical resistance* of the Nichrome wire if its radius was doubled?


[1 mark]

- (b.4) If a potential difference of 10 V is maintained across the Nichrome wire what current will flow in the wire?

[1 mark]

Problem 2: Transformer circuit

(20 Marks)

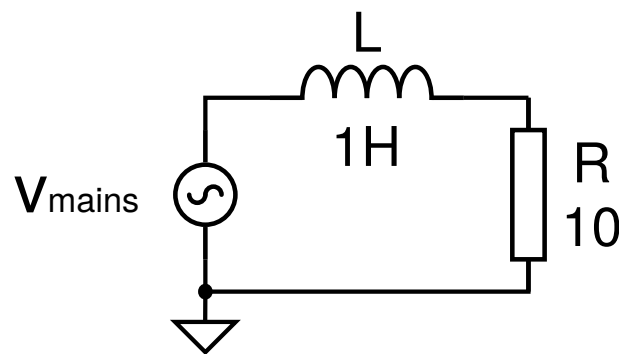

A transformer has a winding that has the equivalent circuit shown in the diagram. The winding is connected to the mains voltage, which has a frequency of 50 Hz and an rms voltage of 230 V.

- What is the impedance of the transformer winding? Express your answer with magnitude and phase and correct units.
[5 marks]
- What current will flow through the winding? Express your answer as both a phasor and also as a function of time. **Hint:** You should assume the mains voltage has zero phase.
[4 marks]
- What are the power factor, the real power and the reactive power in the circuit?
[4 marks]
- Why do we use rms quantities when performing power calculations for ac circuits?
[2 marks]
- We could modify the winding circuit to be resonant by adding a capacitor in series with the resistor and inductor. What capacitor value would we need to use if we wanted to have the resonant frequency be at the mains frequency?
[3 marks]
- Explain qualitatively what we would need to do if we wanted to make a sharper resonance.
[2 marks]