



**Trimester 2
Test 2 – 2022**

ENGR 142

Engineering Physics

Time Allowed: TWO HOURS

CLOSED BOOK

- Permitted materials:**
- 1 hand-written, single-sided, letter-sized A4 equation sheet (with only equations and/or circuit diagrams)
 - non-programmable calculator
 - pencil/pen

Instructions: Answer **All** questions.

Total marks: 60

Charge for an electron: $q_e = 1.6 \times 10^{-19} \text{ C}$.
1 mol = 6.022×10^{23} atoms

Problem 1 (12 marks)

- (a) An aluminium wire has a cross-sectional area equal to $4.0 \times 10^{-6} \text{ m}^2$ and carries a current of 5.0 A. Aluminium has a density of 2.7 g/cm^3 and a molar mass of 27 g/mol. Assume each aluminium atom carries one conduction electron per atom.
- (i) Find the number density of aluminium in units: number of atoms/ m^3 . **(4 marks)**
 - (ii) Find the drift speed of the electrons in the wire. **(2 marks)**
- (b) A tungsten wire 1.5 m long and 0.6 mm in diameter is connected to a source with a potential difference of 1.5 V. At 20°C , 3.5 A of current flows through the wire.
- (i) Find the resistivity of Tungsten at 20°C . **(2 marks)**
 - (ii) Determine the resistivity of Tungsten at 120°C . **(2 marks)**
 - (iii) Find the current in the wire at 120°C . **(2 marks)**

Problem 2 (5 marks)

The quantity of charge, Q (in coulombs), that has passed through a surface of area 2.0 cm^2 varies with time according to the equation:

$$Q(t) = 4t^3 + 5t + 6$$

where t is measured in seconds.

- (a) Find the instantaneous current through the surface at $t = 4.0 \text{ s}$. **(2 marks)**
- (b) Find the average current through the surface from $t = 2.0 \text{ s}$ to $t = 4.0 \text{ s}$. **(2 marks)**
- (c) Find the value of the current density, as a function of time. **(1 mark)**

Problem 3 (13 marks)

(a) The current in the circuit diagram to the right is 2.5 A.

(i) Determine the equivalent resistance in the circuit. **(1 mark)**

(ii) Find the value of the unknown resistor, R . **(2 marks)**

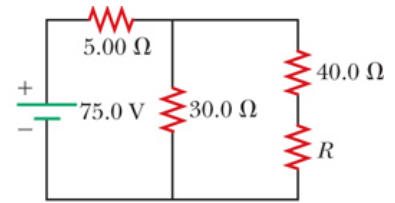


Figure for Problem 3a.

(b) Consider the circuit diagram to the right.

(i) Redraw the circuit diagram, clearly labelling the Kirchoff's loops that you will use to solve the problem. **(1 mark)**

(ii) Using the Kirchoff's loops just drawn and the current directions as given in the problem, solve for the three unknown currents: I_1 , I_2 , and I_3 . **(4 marks)**

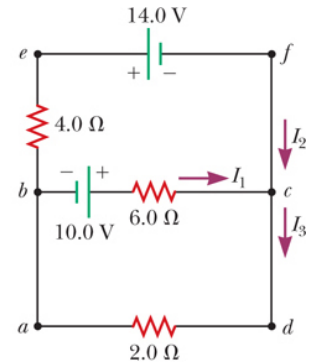


Figure for Problem 3b.

(c) In the circuit diagram to the right, the battery has an emf of 12.0 V, the inductor has an inductance of 3 mH and the capacitor a capacitance of 9.0 pF.

For time $t < 0$, the switch has been set to position a for a long time, so that the capacitor is fully charged. At time $t = 0$, the switch is then thrown to position b , removing the battery from the circuit and connecting the capacitor directly to the inductor.

(i) Find the frequency of the oscillations in the circuit. **(1 mark)**

(ii) Find the equation for the charge as a function of time. **(2 marks)**

(iii) Determine the maximum current that flows in the circuit. **(2 marks)**

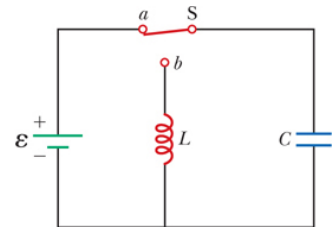


Figure for Problem 3c.

Problem 4 (15 marks)

Consider the circuit shown in the Figure below, where $R = 1000\Omega$, $C = 1\mu\text{F}$ and $L = 1\text{mH}$. The input voltage v_i is $v_i(t) = 100 \cos(1000t + 45^\circ)\text{V}$.

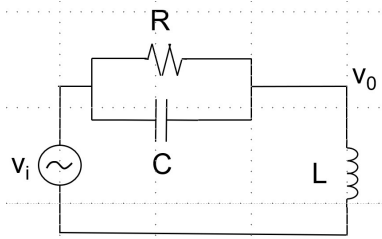


Figure for Problem 4.

- (a) What is the voltage across the inductor? **(8 marks)**
- (c) Sketch the phasor diagram showing: the input voltage, voltage across the inductor, and the current through the inductor. *You do not need to draw the magnitudes to scale.* **(7 marks)**

Problem 5 (7 marks)

- (a) Design a first order filter which attenuates frequencies greater than 100 rad/s by 3 dB relative to the passband. Sketch the circuit diagram and clearly label all components. **(3 marks)**
- (b) For the filter in (a), find the attenuation (in dB) at 500 rad/s . **(4 marks)**

Problem 6 (8 marks)

- (a) Design a filter that passes a band of frequencies 100 rad/s wide centered approximately at 1000 rad/s . Your design should use a $1\ \Omega$ resistor. Sketch the circuit and clearly label all components. **(5 marks)**
- (b) Find the gain (in dB) at the resonant frequency. **(1 mark)**
- (c) Find the exact values of the cut-off frequencies. **(2 marks)**

* * * * *